 


Logic Gates

Gates

Logic gates (or simply gates) are the fundamental building blocks of digital circuitry. As their name implies, they function by “opening” or “closing” to admit or reject the flow of digital information. Gates implement electronically simple logical operations on boolean (Bool’s algebra) variables, i.e. variables that can have only one of two states (0/1, low/high, false/true). In the following figure the accepted electronic symbols for different gates are shown, along with their corresponding “truth tables” and their symbolic logical expressions. All variables (X, A, B, ...) are booleans.




The basic logic gates are AND, NOT, OR, NAND, NOR, XOR.

The most typical logical operations are implemented by AND and OR gates. The logical expression for the AND operation is “if A is true AND B is true then X is true”, and for the OR operation is “if A is true OR B is true then X is true”. The inverted logic AND and OR gates are commonly known as NAND (Not AND) and NOR (Not OR) gates. A XOR (Exclusive-OR) gate implements the logical expression “if A is different than B then X is true”, hence sometimes this gate is called “inequality comparator”.

The buffer and the inverter are not gates but their use is closely associated with them. A buffer doesn't change the logic state of its input. It is only occasionally used for increasing the fan-out, i.e. the capability of the output of one gate to drive a number of other gates. The inverter is much more important and it is used for inverting a logic state, i.e. for performing the logical operation of negation (NOT). The logical expressions for a buffer and an inverter are "X is A" and "X is NOT A", respectively. AND, OR, NAND and NOR gates can have more than 2 inputs.

The **Exclusive-NOR Gate** function or Ex-NOR for short, is a digital logic gate that is the reverse or complementary form of the Exclusive-OR function. The Exclusive-NOR gate is a combination of the Exclusive-OR gate and the NOT gate but has a truth table similar to the standard NOR gate in that it has an output that is normally at logic level "1" and goes "LOW" to logic level "0" when **ANY** of its inputs are at logic level "1".


Ex-NOR Gate Equivalent

 

Diode and Transistor as a switch

The transistor is an amplifier, but can be used as a switch by using the transistor in its saturated region. This can be used to switch a significantly larger current than the input signal. As a switch the transistor is often used to take a signal from a digital circuit and use it to switch larger loads than the integrated circuit (IC) can provide.

The circuit below shows a common simple configuration for a transistor switch circuit. It comprises of one NPN transistor, and depicts two Resistors. The Resistor R_L is not normally a resistor, but represents the resistive value of a device that is being switched. This could be a lamp or relay or some other device that needs a larger current than the input is able to drive directly. The resistor at the base R_b is a resistor used to prevent damage at the base of the transistor. This needs to be large enough to prevent damage to the transistor, but should still allow sufficient current to ensure the transistor switches on. Details of how to determine the size of the resistor are explained below.

 

How the circuit works

For a transistor to act as a switch it needs to be activated as the saturation region. When switched on in saturation the transistor acts almost as a short circuit allowing current through the load.

If the load being switched is an inductive device, such as a motor, solenoid or relay then a diode should be connected in the reverse direction across the load to prevent any back EMF from damaging the transistor.

Logic Families

IC Logic Families:-

Thus far, we have specified the logic level as either 0 or 1, or HIGH or LOW. In circuit implementation, we will have to specify the actual voltage/current levels that constitute a HIGH or a LOW. These standardized voltage/current levels are grouped in families of digital ICs so that ICs belonging to the same family will have the same characteristics.

★ The feature to be concerned of IC logic families:

- fan-out
 - The no. of standard loads can be connected to the output of the gate without degrading its normal operation
 - Sometimes the term *loading* is used for Fan out
- Power dissipation
 - The power needed by the gate
 - Expressed in mW
- Propagation delay
 - The average *transition-delay time* for the signal to propagate from input to output when the binary signal changes in value
- Noise margin
 - The unwanted signals are referred to as *noise*

- Noise margin is the *maximum noise* added to an input signal of a digital circuit that does not cause an undesirable change in the circuit output .
- A *fan-in* of a logic gate is the number of bits that are input to the gate

★ **Fan out:-**

Fan-out is a term that defines the maximum number of digital inputs that the output of a single logic gate can feed. Most transistor-transistor logic (TTL) gates can feed up to 10 other digital gates or devices. Thus, a typical TTL gate has a fan-out of 10.

Characteristics of Ecl

- ★ Nonsaturated digital logic family
- ★ Propagation rate as low as 1-2ns
- ★ Used mostly in high speed circuits
- ★ Noise immunity and power dissipation is the worst of all logic families.
- ★ High level -0.8V, Low level -1.8V
- ★ Including
 - Differential input amplifier
 - Internal temperature and voltage compensated bias network
 - Emitter-follower outputs

Characteristics of CMOS logic:

1. **Dissipates low power:** The power dissipation is dependent on the power supply voltage, frequency, output load, and input rise time. At 1 MHz and 50 pF load, the power dissipation is typically 10 nW per gate.
2. **Short propagation delays:** Depending on the power supply, the propagation delays are usually around 25 nS to 50 nS.
3. **Rise and fall times are controlled:** The rise and falls are usually ramps instead of step functions, and they are 20 - 40% longer than the propagation delays.
4. **Noise immunity** approaches 50% or 45% of the full logic swing.
5. **Levels of the logic signal** will be essentially equal to the power supplied since the input impedance is so high.

Characteristics of TTL logic:

1. **Power dissipation** is usually 10 mW per gate.
2. **Propagation delays** are 10 nS when driving a 15 pF/400 ohm load.
3. **Voltage levels** range from 0 to V_{cc} where V_{cc} is typically 4.75V - 5.25V. Voltage range 0V - 0.8V creates logic level 0. Voltage range 2V - V_{cc} creates logic level 1.

CMOS compared to TTL:

1. CMOS components are typically more expensive than TTL equivalents.
2. CMOS circuits do not draw as much power as TTL circuits while at rest. However, CMOS power consumption increases faster with higher clock speeds than TTL does. Lower current draw requires less power supply distribution, therefore causing a simpler and cheaper design.
3. Due to longer rise and fall times, the transmission of digital signals becomes simpler and less expensive with CMOS chips.
4. CMOS components are more susceptible to damage from electrostatic discharge than TTL components.

Resistor-Transistor Logic (RTL)

Resistor-Transistor Logic (RTL) was invented around 1956. This type of technology, unlike DL, uses active devices such as transistors and therefore can provide inversion. The voltage range goes from 0V for low (0) to 3.5V for high (1). RTL is very inefficient because it dissipates a great amount of power through heat.

RTL has two variants that attempt to improve some of its aspects:

1. When inputs are directly connected to the gate of the BJT, in order to save space and reduce fabrication costs, RTL is known as Direct-Coupled Transistor Logic (DCTL).
2. When capacitors are placed in parallel with input resistors, to speed up operation, RTL is known as Resistor-Capacitor Transistor Logic (RCTL).

Fairchild Semiconductor introduced the first generation of RTL monolithic integrated circuits in either 1962 or 1963. RTL is an obsolete digital logic family.

Diode-Transistor Logic (DTL):-

Diode-Transistor Logic (DTL) was invented in the 1950s. It is a major improvement over DL and RTL because it eliminates signal degradation and reduces power dissipation by means of a transistor which restores digital values and a set of input diodes which replace input resistors.

DTL has two variants that attempt to improve some of its aspects:

1. When a capacitor is placed in parallel with the base resistor and an inductor is placed in series with the collector resistor, DTL is known as Complemented Transistor Diode Logic (CTDL).

2. When a Zener diode and a single power supply are connected to the base of the transistor, DTL is known as High-Threshold Logic (HTL).

Signetics introduced the first generation of DTL monolithic integrated circuits in 1962. DTL was used in the IBM 1401 decimal computer that was delivered in 1959.

Boolean Algebra

The following are a set of basic identities forming a subset of the laws of logic.

Rules of Boolean Algebra

1. A is either 0 or 1
2. Commutative
 1. $A.B = B.A$
 2. $A+B = B+A$
3. Distributive
 1. $A.(B+C) = A.B + A.C$
 2. $A + B.C = (A+B).(A+C)$
4. Identity
 1. $A + 0 = A$
 2. $A + 1 = 1$
 3. $A.1 = A$
 4. $A.0 = 0$
5. Inverse
 1. $A + \text{not}(A) = 1$
 2. $A.\text{not}(A) = 0$
6. De Morgan's Laws
 1. $\text{not}(A+B) = \text{not}(A).\text{not}(B)$
 2. $\text{not}(A.B) = \text{not}(A) + \text{not}(B)$

Karnaugh Maps

1. A **Karnaugh Map** (sometimes called K-map) for a Boolean function $f(x_1, x_2, \dots, x_n)$ is a rectangular grid of size $2^k \times 2^{n-k}$ constructed as follows.
2. k is equal to $n/2$
3. Rows represent truth assignments for k variables x_1, x_2, \dots, x_k and are labeled with conjunction of literals corresponding to the truth assignments for the rows.
4. The Hamming distance between the truth assignments of consecutive rows is always equal to 1.
5. Columns represent truth assignments for $(n-k)$ variables $x_{k+1}, x_{k+2}, \dots, x_n$ and are labeled with conjunction of literals corresponding to the truth assignments for the columns.

6. The Hamming distance between the truth assignments of consecutive columns is always equal to 1.
7. Each cell on a column and a row is 1 if the Boolean function $f(x_1, x_2, \dots, x_n)$ is equal to 1 for the truth assignment represented by the column and the row. The cell has a symbol "X" (called "don't care") if a value of the Boolean function doesn't matter. Otherwise, the cell is empty.

Minimal Sum

A sum of products (SOP) expression such that no SOP expression for Y has fewer product terms and any SOP expression with the same number of product terms has at least as many literals.

UNIT -II

NUMBER SYSTEM

A number system of base (also called radix) r is a system, which has r distinct symbols for r digits. A number is represented by a string of these symbolic digits. To determine the quantity that the number represents, we multiply the number by an integer power of r depending on the place it is located and then find the sum of weighted digits.

Binary-coded decimal (BCD) is a digital encoding method for numbers using decimal notation, with each decimal digit represented by its own binary sequence. In BCD, a numeral is usually represented by four bits which, in general, represent the decimal range 0 through 9.

Examples:

Convert decimal 4019 to BCD

4 0 1 9

0100 0000 0001 1001

The BCD equivalent of $(4019)_{10}$ is 0100 0000 0001 1001

Convert BCD number 0001 1001 0000 0111 to decimal

0001 1001 0000 0111

1 9 0 7

The decimal equivalent of BCD Number 0001 1001 0000 0111 is $(1907)_{10}$. BCD numbers are useful wherever decimal information is transferred into a computer. The pocket calculator is one of the best examples for the application of BCD numbers. Other examples of BCD system are electronic counters, digital voltmeter and digital clocks.

Octal to Binary

Converting from octal to binary is as easy as converting from binary to octal. Simply look up each octal digit to obtain the equivalent group of three binary digits.

Octal: 0 1 2 3 4 5 6 7

Binary: 000 001 010 011 100 101 110 111

Octal = 3 4 5

Binary = 011 100 101 = 011100101 binary

Octal to Hexadecimal

When converting from octal to hexadecimal, it is often easier to first convert the octal number into binary and then from binary into hexadecimal. For example, to convert 345 octal into hex:

(from the previous example)

Octal = 3 4 5

Binary = 011 100 101 = 011100101 binary

Drop any leading zeros or pad with leading zeros to get groups of four binary digits (bits):

Binary 011100101 = 1110 0101

Octal to Decimal

Converting octal to decimal can be done with repeated division.

1. Start the decimal result at 0.
2. Remove the most significant octal digit (leftmost) and add it to the result.
3. If all octal digits have been removed, you're done. Stop.
4. Otherwise, multiply the result by 8.
5. Go to step 2.

Octal Digits	Operation	Decimal Result	Operation	Decimal Result
345	+3	3	$\times 8$	24
45	+4	28	$\times 8$	224
5	+5	229	done.	

The conversion can also be performed in the conventional mathematical way, by showing each digit place as an increasing power of 8.

$$345_{\text{octal}} = (3 * 8^2) + (4 * 8^1) + (5 * 8^0) = (3 * 64) + (4 * 8) + (5 * 1) = 229_{\text{decimal}}$$

Hexadecimal to Binary

Converting from hexadecimal to binary is as easy as converting from binary to hexadecimal. Simply look up each hexadecimal digit to obtain the equivalent group of four binary digits.

Hexadecimal: 0 1 2 3 4 5 6 7

Binary: 0000 0001 0010 0011 0100 0101 0110 0111

Hexadecimal: 8 9 A B C D E F

Binary: 1000 1001 1010 1011 1100 1101 1110 1111

Hexadecimal = A 2 D E

Binary = 1010 0010 1101 1110 = 1010001011011110 binary

Hexadecimal to Octal

When converting from hexadecimal to octal, it is often easier to first convert the hexadecimal number into binary and then from binary into octal. For example, to convert A2DE hex into octal:

(from the previous example)

Hexadecimal = A 2 D E

Binary = 1010 0010 1101 1110 = 1010001011011110 binary

Add leading zeros or remove leading zeros to group into sets of three binary digits.

Binary: 1010001011011110 = 001 010 001 011 011 110

Then, look up each group in a table:

Binary: 000 001 010 011 100 101 110 111

Octal: 0 1 2 3 4 5 6 7

Binary = 001 010 001 011 011 110

Octal = 1 2 1 3 3 6 = 121336 octal

Therefore, through a two-step conversion process, hexadecimal A2DE equals binary 1010001011011110 equals octal 121336.

Hexadecimal to Decimal

Converting hexadecimal to decimal can be performed in the conventional mathematical way, by showing each digit place as an increasing power of 16. Of course, hexadecimal letter values need to be converted to decimal values before performing the math.

Hexadecimal: 0 1 2 3 4 5 6 7

Decimal: 0 1 2 3 4 5 6 7

Hexadecimal: 8 9 A B C D E F

Decimal: 8 9 10 11 12 13 14 15

A2DE hexadecimal:

$$\begin{aligned} &= ((A) * 16^3) + (2 * 16^2) + ((D) * 16^1) + ((E) * 16^0) \\ &= (10 * 16^3) + (2 * 16^2) + (13 * 16^1) + (14 * 16^0) \\ &= (10 * 4096) + (2 * 256) + (13 * 16) + (14 * 1) \\ &= 40960 + 512 + 208 + 14 \\ &= 41694 \text{ decimal} \end{aligned}$$

EXCESS – 3 CODE:

The Excess-3 code is a decimal code that has been used in older computers. This is an un-weighted code. Its binary code assignment is obtained from the corresponding BCD equivalent binary number after the addition of binary 3 (0011).

<u>DECIMAL</u>	<u>BCD</u>
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	0001 0000

EXCESS 3 CODE

0011

0100

0101

0110

0111

1000

1001

1010

1011

1100

0100 0011

GRAY CODE

This is a variable weighted code and is cyclic. This means that it is arranged so that every transition from one value to the next value involves only one bit change. The gray code is sometimes referred to as reflected binary, because the first eight values compare with those of the last 8 values, but in reverse order.

Decimal	Binary	Gray
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100

The gray code is often used in mechanical applications such as shaft encoders.

Arithmetic

This is binary addition with the carry ignored.

Converting Gray Code to Binary

A. write down the number in gray code

B. the most significant bit of the binary number is the most significant bit of the gray code

C. add (using modulo 2) the next significant bit of the binary number to the next significant bit of the gray coded number to obtain the next binary bit

D. repeat step C till all bits of the gray coded number have been added modulo 2
the resultant number is the binary equivalent of the gray number

9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

Parity generation and Checking:-

A parity generator checks the data to be transmitted and outputs a 0 (parity bit) if the number of logic 1's in the data is even, and a logic 1 if the number is odd. So a checker takes the transmitted data and the parity bit and will compare the two, and if they are both of the same logic then the you can conclude that the data was received successfully (i.e no bits were lost during transmission). Parity checker/generator use the exact same devices, but with one comparing instead of generating.

Half-Adder


It computes the sum of two single bits x and y by producing the sum bit s and the carry bit c.

	x	y			
+	x	y		u	v
cs	0	0		0	0
		0		0	1
		1		0	1
		1		1	0

Design

$$c = x \cdot y$$

 
$$s = \overline{x} \cdot \overline{y} + x \cdot y$$



Full-Adder

It computes the sum of two single bits x and y and a carry c_{in} from the lower-order bit, by producing the sum bit s and the carry bit c_{out} to the higher-order bit.

x	y	c_{in}		c_{out}	s
0	0	0		0	0
0	0	1		0	1
0	1	0		0	1
0	1	1		1	0
1	0	0		0	1
1	0	1		1	0
1	1	0		1	0
1	1	1		1	1

 

Subtractor : Subtractor is the one which used to subtract two binary number and provides Difference and Borrow as a output. basically we have two types of subtractor.

Half Subtractor

Full Subtractor


Half Subtractor :Half Subtractor is used for subtracting one single bit binary number from another single bit binary number. The truth table of Half Subtractor is shown below.

Half Subtractor-Truth Table			
Input		Output	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0
www.flintgroups.com			

$$\text{Difference} = A'B + AB' = A \oplus B$$

Borrow= $A'B$

 The logic Diagram of Half Subtractor is shown below.



Full Subtractor : A logic Circuit Which is used for Subtracting Three Single bit Binary numbers is known as Full Subtractor. The Truth Table of Full Subtractor is Shown Below.

Full Subtractor-Truth Table				
Input			Output	
A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1
www.flintgroups.com				

From the Truth Table The Difference and Borrow will written as

$$\text{Difference} = A'B'C + A'BB' + AB'C' + ABC$$

Reduce it like adder

Then We got

$$\text{Difference} = A \oplus B \oplus C$$


$$\text{Borrow} = A'B'C + A'BC' + A'BC + ABC$$

$$= A'B'C + A'BC' + A'BC + A'BC + A'BC + ABC \quad \text{----->} \quad A'BC = A'BC + A'BC + A'BC$$

$$=A'C(B'+B)+A'B(C'+C)+BC(A'+A)$$

$$\text{Borrow}=A'C+A'B+BC$$

 
The logic diagram of Full Subtractor is Shown below



Full Subtractor-Logic Diagram

Parallel Binary Adder/subtractor

The use of one half-adder or one full-adder alone are great for adding up two binary numbers with a length of one bit each, but what happens when the computer needs to add up two binary numbers with a longer length. The fastest way by far is to use the Parallel Binary Adder. The parallel binary adder uses one half-adder, along with one or more full adders. The number of total adders needed depends on the length of the largest of the two binary numbers that are to be added. For example, if we were to add up the binary numbers 1011 and 1, we would need four adders in total, because the length of the larger number is four. here is a demonstration of how a four-bit parallel binary adder works, using 1101 and 1011 as the two numbers to add. The parallel binary subtractor is same as parallel binary adder only the difference is this that in subtractor we use borrow inspite of giving carry to another bit.

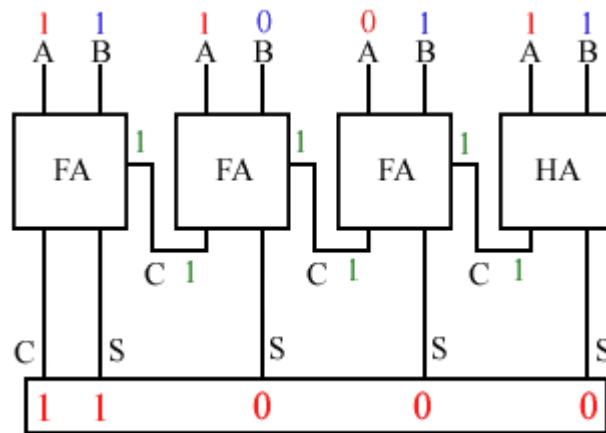

Just like when we add without the computer, in the parallel binary adder, the computer adds from right to left. Here is a step by step list, showing that what happens in the parallel Binary Adder

1	In the only half-adder, inputs of 1 and 1 give us 0 with a carry of 1.
2	In the first full-adder (going from right to left), the inputs of 1 and 0 plus the carry of 1 from the half-adder give us a 0 with a carry of 1.
3	In the second full adder, the inputs of 0 and 1 plus the carry of 1 from the previous full-adder give us a 0 with a carry of 1.
4	In the third and final full adder, the inputs of 1 and 1 plus the carry of 1 from the previous full-adder give us a 1 with a carry of 1.


5	Since there are no more numbers to add up, and there is still a carry of 1, the carry becomes the most significant bit.
6	The sum of 1101 and 1011 is 11000.

Parallel Binary Multiplier/ divider:

A binary multiplier is an electronic circuit used in digital electronics, such as a computer, to multiply two binary numbers. It is built using binary adders. A binary computer does exactly the same, but with binary numbers. In binary encoding each long number is multiplied by one digit (either 0 or 1), and that is much easier than in decimal, as the product by 0 or 1 is just 0 or the same number. Therefore, the multiplication of two binary numbers comes down to calculating partial products (which are 0 or the first number), shifting them left, and then adding them together.

A variety of computer arithmetic techniques can be used to implement a digital multiplier. Most techniques involve computing a set of partial products, and then summing the partial products together. This process is similar to the method taught to primary schoolchildren for conducting long multiplication on base-10 integers, but has been modified here for application to a base-2 (binary) numeral system. This is much simpler than in the decimal system, as there is no table of multiplication to remember: just shifts and adds. This method is mathematically correct and has the advantage that a small CPU may perform the multiplication by using the shift and add features of its arithmetic logic unit rather than a specialized circuit. The method is slow, however, as it involves many intermediate additions. These additions take a lot of time. Faster multipliers may be engineered in order to do fewer additions; a modern processor can multiply two 64-bit numbers with 6 additions (rather than 64), and can do several steps in parallel.

 
The process is same as for Parallel Divider also.



Encoder :-


Encoder is a circuit which converts the analog signal in to the digital signal. An encoder is a device, circuit, transducer, software program, algorithm or person that converts information from one format or code to another, for the purposes of standardization, speed, secrecy, security, or saving space by shrinking size.

Encoder Circuit Diagram

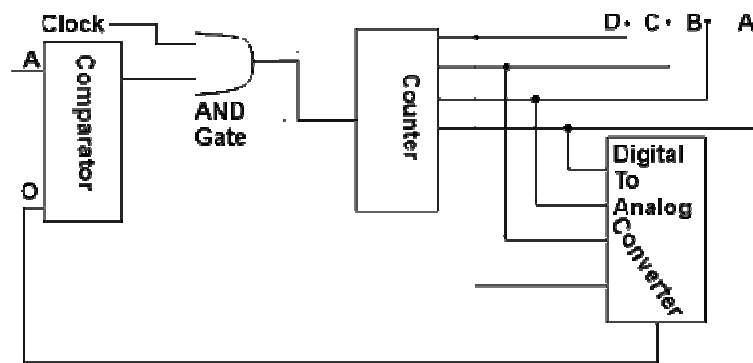

Decoder:-

A decoder is a device which does the reverse operation of an encoder, undoing the encoding so that the original information can be retrieved. The same method used to encode is usually just reversed in order to decode. It is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines. Decoding is necessary in applications such as data multiplexing, 7 segment display and memory address decoding.

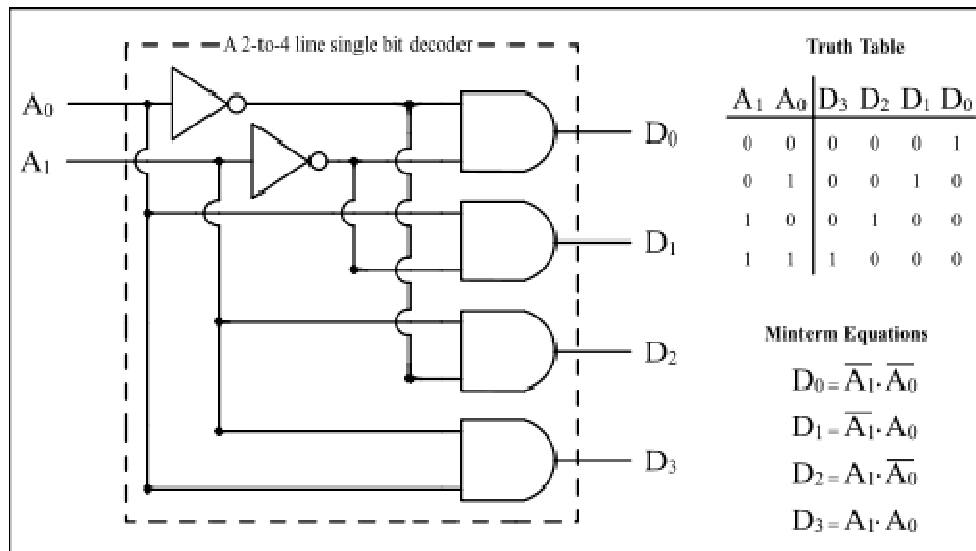

The example decoder circuit would be an AND gate because the output of an AND gate is "High" (1) only when all its inputs are "High." Such output is called as "active High output". If instead of AND gate, the NAND gate is connected the output will be "Low" (0) only when all its inputs are "High". Such output is called as "active low output".

Multiplexers:-

Multiplexer (or MUX) is a device that selects one of several analog or digital input signals and forwards the selected input into a single line. A multiplexer of 2^n inputs has n select lines, which are used to select which input line to send to the output. Multiplexers are mainly used to increase the amount of data that can be sent over the network within a certain amount of time and bandwidth. A multiplexer is also called a data selector. An electronic multiplexer makes it possible for several signals to share one device or resource, for example one A/D converter or one communication line, instead of having one device per input signal. On the other hand, a **demultiplexer** (or demux) is a device taking a single input signal and selecting one of many data-output-lines, which is connected to the single input. A multiplexer is often used with a complementary demultiplexer on the receiving end. An electronic multiplexer can be considered as a multiple-input, single-output switch, and a demultiplexer as a single-input, multiple-output switch.

De-Multiplexer:-


The demultiplexer is the inverse of the multiplexer, in that it takes a data input and n address inputs. It has $2n$ outputs. The address input determine which data output is going to have the same value as the data input. The other data outputs will have the value 0.

UNIT-III

Flip Flop:-

A flip-flop or latch is a circuit that has two stable states and can be used to store state information. The circuit can be made to change state by signals applied to one or more control inputs and will have one or two outputs. It is the basic storage element in sequential logic. Flip-flops and latches are a fundamental building block of digital electronics systems used in computers, communications, and many other types of systems.

Flip-flops and latches are used as data storage elements. Such data storage can be used for storage of state, and such a circuit is described as sequential logic. When used in a finite-state machine, the output and next state depend not only on its current input, but also on its current state (and hence, previous inputs). It can also be used for counting of pulses, and for synchronizing variably-timed input signals to some reference timing signal.

 


(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(b) Truth table

Basic flip-flop circuit with NOR gates

 

S.R Flip Flop:- When using static gates as building blocks, the most fundamental latch is the simple SR latch, where S and R stand for set and reset. It can be constructed from a pair of cross-coupled NOR logic gates. The stored bit is present on the output marked Q.

While the S and R inputs are both low, feedback maintains the Q and Q' outputs in a constant state, with Q the complement of Q'. If S (Set) is pulsed high while R (Reset) is held low, then the Q output is forced high, and stays high when S returns to low; similarly, if R is pulsed high while S is held low, then the Q output is forced low, and stays low when R returns to low. The R = S = 1 combination is called a restricted combination or a forbidden state because, as both NOR gates then output zeros, it breaks the logical equation $Q = \text{not } Q'$. The combination is also inappropriate in circuits where both inputs may go low simultaneously (i.e. a transition from restricted to keep). The output would lock at either 1 or 0 depending on the propagation time relations between the gates (a race condition). In certain implementations, it could also lead to longer ringings (damped oscillations) before the output settles, and thereby result in undetermined values (errors) in high-frequency digital circuits. Although this condition is usually avoided, it can be useful in some applications.

To overcome the restricted combination, one can add gates to the inputs that would convert (S,R) = (1,1) to one of the non-restricted combinations. That can be:

- Q = 1 (1,0) – referred to as an S-latch
- Q = 0 (0,1) – referred to as an R-latch
- Keep state (0,0) – referred to as an E-latch


Alternatively, the restricted combination can be made to toggle the output. The result is the JK latch.

J-K FlipFlop:-


A JK flip-flop is a refinement of the SR flip-flop in that the indeterminate state of the SR type is defined in the JK type. Inputs J and K behave like inputs S and R to set and clear the flip-flop (note that in a JK flip-flop, the letter J is for set and the letter K is for clear). When logic 1 inputs are applied to both J and K simultaneously, the flip-flop switches to its complement state, i.e., if $Q=1$, it switches to $Q=0$ and vice versa.

A clocked JK flip-flop is shown in Figure below. Output Q is ANDed with K and CP inputs so that the flip-flop is cleared during a clock pulse only if Q was previously 1. Similarly, output Q' is ANDed with J and CP inputs so that the flip-flop is set with a clock pulse only if Q' was previously 1.

Note that because of the feedback connection in the JK flip-flop, a CP signal which remains a 1 (while $J=K=1$) after the outputs have been complemented once will cause repeated and continuous transitions of the outputs. To avoid this, the clock pulses must have a time duration less than the propagation delay through the flip-flop. The restriction on the pulse width can be eliminated with a master-slave or edge-triggered construction. The same reasoning also applies to the T flip-flop presented next.

 

(a) Logic diagram

 

(b) Graphical symbol

Q	J	K	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

(c) Transition table

RACE AROUND CONDITION:-

Let us consider a JK Flip Flop (Hereby called FF). The excitation table of this FF is as follows :

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$Q_n^{\text{Bar}} \sim \text{Complement of } Q_n$


Let us say that a clock of certain frequency is fed to the FF, and consider the case of $J=K=1$, and the propagation delay of FF is very very less than the clock pulse time

Then the FF continues complementing the output an unpredictable number of times, thus leading to anomaly in the final output after the pulse time of the clock is completed


This condition is called Race Around condition and can be avoided by using a Master-Slave JK FF

T Flip-Flop:-

 The T flip-flop is a single input version of the JK flip-flop. As shown in Figure below, the T flip-flop is obtained from the JK type if both inputs are tied together. The output of the T flip-flop "toggles" with each clock pulse.



(a) Logic diagram

 


(b) Graphical symbol

Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0


Master-Slave Flip-Flop

A master-slave flip-flop is constructed from two separate flip-flops. One circuit serves as a master and the other as a slave. The logic diagram of an SR flip-flop is shown in diagram. The master flip-flop is enabled on the positive edge of the clock pulse CP and the slave flip-flop is disabled by the inverter. The information at the external R and S inputs is transmitted to the master flip-flop. When the pulse returns to 0, the master flip-flop is disabled and the slave flip-flop is enabled. The slave flip-flop then goes to the same state as the master flip-flop.

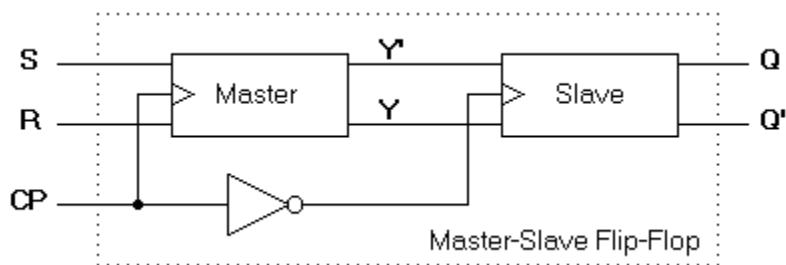

Logic diagram of a master-slave flip-flop

The timing relationship is shown in diagram and is assumed that the flip-flop is in the clear state prior to the occurrence of the clock pulse. The output state of the master-slave flip-flop occurs on the negative transition of the clock pulse. Some master-slave flip-flops change output state on the positive transition of the clock pulse by having an additional inverter between the CP terminal and the input of the master.

 


Timing relationship in a master slave flip-flop

D Flip Flop:-

This latch exploits the fact that in the two active input combinations (01 and 10) of a gated SR latch R is the complement of S. The input NAND stage converts the two D input states (0 and 1) to these two input combinations for the next SR latch by inverting the data input signal. The low state of the enable signal produces the inactive "11" combination. Thus a gated D-latch may be considered as a one-input synchronous SR latch. This configuration prevents from applying the restricted combination to the inputs. It is also known as transparent latch, data latch, or simply gated latch. It has a data input and an enable signal (sometimes named clock, or control). The word transparent comes from the fact that, when the enable input is on, the signal propagates directly through the circuit, from the input D to the output Q.

 Transparent latches are typically used as I/O ports or in asynchronous systems, or in synchronous two-phase systems (synchronous systems that use a two-phase clock), where two latches operating on different clock phases prevent data transparency as in a master–slave flip-flop..



Gated D latch truth table

E/C	D	Q	Q	Comment
0	X	Q _{prev}	Q _{prev}	No change
1	0	0	1	Reset
1	1	1	0	Set


The truth table

shows that when the enable/clock input is 0, the D input has no effect on the output. When E/C(Enable clock) is high, the output equals D.

Clocked SR Flip-Flop

The clocked SR flip-flop shown in diagram consists of a basic NOR flip-flop and two AND gates. The outputs of the two AND gates remain at 0 as long as the clock pulse (or CP) is 0, regardless of the S and R input values. When the clock pulse goes to 1, information from the S

 and R inputs passes through to the basic flip-flop. With both $S=1$ and $R=1$, the occurrence of a clock pulse causes both outputs to momentarily go to 0. When the pulse is removed, the state of the flip-flop is indeterminate, i.e., either state may result, depending on whether the set or reset input of the flip-flop remains a 1 longer than the transition to 0 at the end of the pulse.



(a) Logic diagram

Q	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	indeterminate
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	indeterminate

(b) Truth table

Realisation of one flip-flop using other flip-flop.

Any flip-flop can be implemented as combinational logic for the next state function in conjunction with a flip-flop of another type.

 


Figure 6.40 D flip-flop implemented by J-K flip-flop and J-K flip-flop implemented by D flip-flop

As an example, Figure shows how to implement a D flip-flop with a $J-K$ flip-flop and, correspondingly, a $J-K$ flip-flop with a D flip-flop.

Consider the leftmost circuit. If D is 1, we place the $J-K$ flip-flop in its set input configuration ($J = 1, K = 0$). If D is 0, $J-K$'s inputs are configured for reset ($J = 0, K = 1$). In the case of the

rightmost circuit, the D flip-flop's input is driven with logic that implements the characteristic equation for the J - K flip-flop, namely $J\bar{Q} + KQ$.

General Procedure We can follow a general procedure to map among the different kinds of flip-flops. It is based on the concept of an excitation table, that is, a table that lists all possible state transitions and the values of the flip-flop inputs that cause a given transition to take place.

Q	Q'	R	S	J	K	T	D
0	0	X	0	0	X	0	0
0	1	0	1	1	X	1	1
1	0	1	0	X	1	1	0
1	1	0	X	X	0	0	1

Figure 6.11 Excitation tables for R - S , J - K , T , and D flip-flops

Figure gives excitation tables for R - S , J - K , T , and D flip-flops. If the current state is 0 and the next state is to be 0 too, then the first row of the table describes the flip-flop input to cause that state transition to take place. If an R - S latch is being used, it doesn't matter what value is placed on R as long as S is left unasserted. $R = 0$, $S = 0$ holds the current state at 0; $R = 1$, $S = 0$ resets the state to 0. The effect is the same.

If we are using a J - K flip-flop, the transition from 0 to 0 is accomplished by ensuring that J is left unasserted. The value of K does not matter. If $J = 0$, $K = 0$, the current state is held at 0; if $J = 0$, $K = 1$, the state is reset to 0.

If we are using a T flip-flop, the transition does not change the current state, so the input should be 0. If a D flip-flop is used, we set the input to the desired next state, which is 0 in this case. The same kind of analysis can be applied to complete the excitation table for the three other cases.

A flip-flop's next state function can be written as a K -map. For example, the next state K -map for the D flip-flop is shown in Figure (a).

Q/D	0	1
0	0	1
1	0	1

$$Q^+ = D$$

(a) K-map for D flip-flop and character is the equation

Q/D	0	1
0	0	1
1	X	X

$$J = D$$

Q/D	0	1
0	X	X
1	1	0

$$K = D$$

(b) K-maps for J and K inputs

Figure 6.4-2 Implementing a given flip-flop by one of another type.

To realize a D flip-flop in terms of a J - K flip-flop, we simply remap the state transitions implied by the D flip-flop's K -map into equations for the J and K inputs. In other words, we express J and K as functions of the current state and D .

The procedure works as follows. First we draw K -maps for J and K , as in Figure (b). Then we fill them in the following manner. When $D = 0$ and $Q = 0$, the next state is 0. The excitation table tells us that the inputs to J and K should be 0 and X, respectively, if we desire a 0-to-0 transition. These values are placed into corresponding entries of the J and K K -maps. The inputs $D = 0$, $Q = 1$ lead to a next state of 0. This is a 1-to-0 transition, and J and K should be X and 1, respectively. For $D = 1$, $Q = 0$, the transition is from 0 to 1, and J must be 1 and K should be X. The final transition, $D = 1$, $Q = 1$, is from 1 to 1, and J and K are X and 0. A quick look at the K -maps confirms that $J = D$ and $K = D$.

The implementation of a J - K flip-flop by a D flip-flop follows the same procedure. We start with a K -map to describe the next state in terms of the three variables J , K , and the current state Q . To obtain the transition from 0 to 0 or 1 to 0 requires that D be 0; similarly, D must be 1 to implement a 0-to-1 or 1-to-1 transition. In other words, the function for D is identical to the next state. The equation for D can be read directly from the next state K -map for the J - K flip-flop:

$$D = J + KQ$$

This K -map is shown in Figure.

	\overline{Q}		Q	
	\overline{Q}		Q	
	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$Q^+ = D = \overline{Q} + KQ$$

Figure 6.43 K-map for J-K Flip

Applications of Flip Flops

Flip flops are used in digital electronics some of its main applications are described below.

1) Data Storage

A flip flop can store one bit at a time in digital circuit. In order to store more than one bit flip flop can be connected in series and parallel called registers. A register is simply a data storage device for a number of bits in which each flip flop store one bit of information (0 or 1). Thus a 4 bit register consists of 4 individual flip flops, each able to store one bit of information at a time.

 


Figure 1: Bit Binary Register

Figure 1 shows a 4 bit register. Any number from $(0000)_2$ to $(1111)_2$ may be stored in it simply by setting or resetting the appropriate flip flops. Let us suppose that flip flop one is SET(1), Flip flop 2 is RESET(0), flip flop 3 is RESET(0) and flip flop 4 is SET(1), the binary number stored in this register is $(1001)_2$.

2) Data Transfer

Flip flops can also be used extensively to transfer the data. For this purpose shift register is used. A shift register is a register which is able to shift or transfer its content within itself without changing the order of the bits. It may be designed to shift or transfer data either left or right. The data is shifted or transferred one bit at a time, when a clock pulse is applied. The shift register can be used for temporary storage of data. The shift register is used for multiplication and division where bit shifting is required. The shift register can be built using RS, JK or D flip flops.

A four stage shift right register is shown in Figure 2. Input data is applied to store D and shifted right.

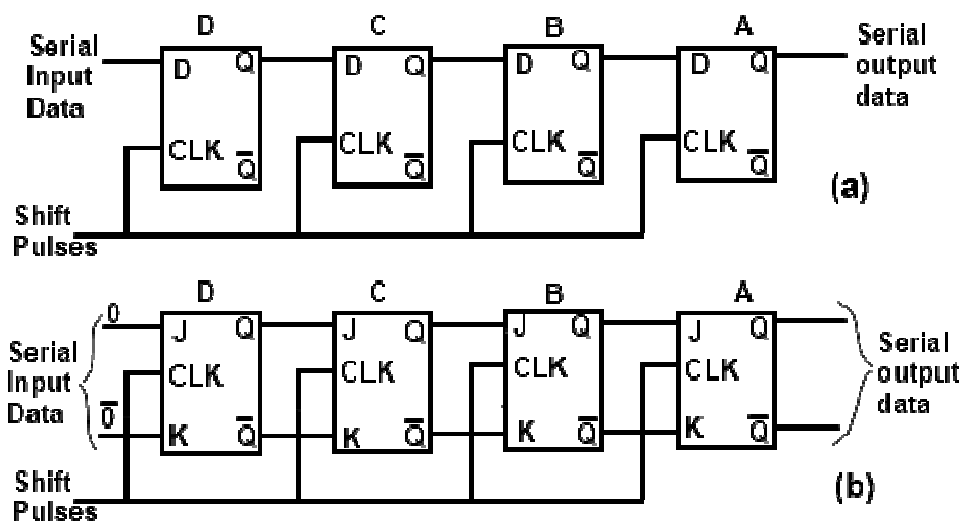


Figure 2: Shift Right Register

Each flip flop is controlled by the output of the preceding flip flop. Clock signal is applied simultaneously to all flip flops. With each clock pulse information is transferred to next flip flop as shown below.

D	C	B	A
0	0	0	0

1011 After 1st Clock

1	0	0	0
---	---	---	---

1	1	0	0
0	1	1	0
1	0	1	1

In the above four bit shift right the information from input could be transferred to output in four clock pulses. This is an example of data transfer.

3) Counter

Another major application of flip flops is a digital counter. It is used to count pulses or events and it can be made by connecting a series of flip flops. Counter can count up to 2^n . Where n is the number of flip flops. Figure 3 shows a simplest binary ripple counter made by flip flops. It consists of connections of flip flop without any logic gate. Each flip flop is triggered by the output of its proceeding flip flop.

 


Figure 3: Four stage Counter

They are used in digital equipments, clocks, frequency counters and computers etc.

4) Frequency Division

Flip flops can divide the frequency of periodic waveform. When a pulse wave is used to toggle an flip flop, the output frequency becomes one half the input frequency, as shown in Figure 4

 


Figure 4: JK Flip Flop Used as A Frequency Division

The output of each flip flop is half the frequency of an input. If the input frequency is 160 KHz then output of each flip flop would be so after first flip flop, 80 after second flip flop and 40 after third flip flop.

Input frequency 160 KHz

Frequency of first flip flop 80 KHz

Frequency of 2nd flip flop 40 KHz

Frequency of 3rd flip flop 20 KHz


Shift Registers

A register is a device which is used to store information. Flip flops are often used to make a register. Each flip flop can store 1-bit of information and therefore for storing a n-bit word n-flip-flops are required in the register for example a computer employing 16-bit word length requires 16 flip-flops to hold the number before it is manipulated. The input to a register or output from it may be either in serial or parallel form depending upon the requirement. If in these registers the connection is done in such a way that the output of one of the flip flop forms in input to other, it is known as a shift register. The data in a shift register is moved serially (one bit at a time). The shift register can be built using RS, JK or D flip-flops.

Types of Shift Register:-


Serial-In Serial-Out

 This configuration allows conversion from serial to Serial format. Data are input serially, and once the data has been input, it received Serially at the Output.



Serial-In, Parallel-Out

 This configuration allows conversion from serial to parallel format. Data are input serially, and once the data has been input, it may be either read off at each output simultaneously, or it can be shifted out and replaced.



Parallel-In, Serial-Out

This configuration has the data input in parallel format. To write the data to the register, the Write/Shift control line must be held LOW. To shift the data, the control line is brought HIGH and the registers are clocked. As long as the number of clock cycles is not more than the length of the data-string, the Data Output, Q, will be the parallel data read off in order.

Parallel-In, Parallel-Out

This kind of shift register takes the data from the parallel inputs (D0-D3) and shifts it to the corresponding output (Q0-Q3) when the registers are clocked. It can be used as a kind of 'history', retaining old information as the input in another part of the system, until ready for new information, whereupon, the registers are clocked, and the new data are 'let through'

Bidirectional Shift Register

A bidirectional shift register is one which can do both the shift left and shift right operations. The following steps are controlled by a clock sequentially. The lower register is the one in which the data being shifted right or left. The upper register is being used as a temporary storage. The steps are as follows.

1. The contents of the lower register are gated up directly to the upper register, which is assumed to have been cleared previously. This is a parallel transfer of data and is achieved by the first pulse or gate up pulse applied as the gate up terminals.
2. All the lower registers are reset i.e. set =0 by giving a pulse at the reset terminals.
3. The contents of the upper register are gate down to the lower register either one position to the right or to the left as desired. This is again a parallel transfer of data.
4. The upper register is reset for the next shift operation.

UNIT -IV

Counters

COUNTERS

A counter is a device used to count operations, quantities, or periods of time. Counting is frequently required in digital computers and other digital systems to record the number of events occurring in a specified interval of time. Normally an electronic counter is used for counting the number of pulses coming at the input line in a specified time period. The counter must possess memory since it has to remember its past states. As with other sequential logic circuits counters can be synchronous or asynchronous. As the name suggests, it is a circuit which counts. The main purpose of the counter is to record the number of occurrence of some input. There are many types of counter both binary and decimal. Commonly used counters are

- 1) Ripple counter
- 2) Synchronous Counter
- 3) Modulo Counters
- 4) Ring Counter
- 5) Twisted Ring Counter


1) **Ripple counter:-**

- The first flip-flop is clocked by the external clock pulse, and then each successive flip-flop is clocked by the Q or Q' output of the previous flip-flop.
- But counters with states less than this number are also possible.
- They are designed to have the number of states in their sequences, which are called truncated sequences.
- These sequences are achieved by forcing the counter to recycle before going through all of its normal states.

 2) **Synchronous Counters** - If all flip flops in the counter are triggered by a common clock pulse, then the counter is called a "synchronous counter" and all memory elements are simultaneously triggered by the same clock

Ring Counter

The ring counter is the simplest example of a shift register. The simplest counter is called a Ring counter. The ring counter contains only one logical 1 or 0 which it circulates. The total cycle length is equal to the number of stages. The ring counter is useful in applications where count has to be recognized in order to perform some other logical operation. Since only one output is ever at logic 1 at given time extra logic gates are not required to decode the counts and the flip flop outputs may be used directly to perform the required operation.




Simple Ring Counter

Counter Truth Table

Clock	0 ₁	0 ₂	0 ₃	0 ₄
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	1	0	0	0

Johnson Counter (Twisted Ring counter)

A Johnson counter is a modified ring counter, where the inverted output from the last flip flop is connected to the input to the first. The register cycles through a sequence of bit-patterns. The MOD of the Johnson counter is $2n$ if n flip-flops are used. The main advantage of the Johnson counter is that it only needs half the number of flip-flops compared to the standard ring counter for the same MOD.

 


Johnson counter (note the \overline{Q}_D to D_A feedback connection)

Modulo Counter:

A counter is a device which stores (and sometimes displays) the number of times a particular event or process has occurred, often in relationship to a clock signal.

Decade counter (Modulo Counter)

 

A circuit diagram of decade counter using JK FlipFlops (74LS112D)

A decade counter is one that counts in decimal digits, rather than binary. A decade counter may have each digit binary encoded (that is, it may count in binary-coded decimal, as the 7490 integrated circuit did) or other binary encodings (such as the bi-quinary encoding of the 7490 integrated circuit). Alternatively, it may have a "fully decoded" or one-hot output code in which each output goes high in turn (the 4017 is such a circuit). The latter type of circuit finds applications in multiplexers and demultiplexers, or wherever a scanning type of behavior is useful. Similar counters with different numbers of outputs are also common.

The decade counter is also known as a mod-counter when it counts to ten (0, 1, 2, 3, 4, 5, 6, 7, 8, 9). A Mod Counter that counts to 64 stops at 63 because 0 counts as a valid digit.

Primary Storage

RAM Memory

Random Access Memory (RAM) is the best known form of *Computer Memory*. The Read and write (R/W) memory of a computer is called RAM. The User can write information to it and read information from it. The RAM is a volatile memory; it means information written to it can be accessed as long as power is on. As soon as the power is off, it cannot be accessed..RAM holds data and processing instructions temporarily until the CPU needs it.

RAM is considered “**random access**” because we can access any memory cell directly if we know the row and column that intersect at that cell.

There are two basic types of RAM :

- (i) Dynamic Ram
- (ii) Static RAM

Dynamic RAM : loses its stored information in a very short time (for milli sec.) even when power supply is on. D-RAM's are cheaper & lower.

Static RAM uses a completely different technology. S-RAM retains stored information only as long as the power supply is on. Static RAM's are costlier and consume more power. They have higher speed than D-RAMs.

ROM Memory

Read only memory: Its non volatile memory, i.e, the information stored in it, is not lost even if the power supply goes off. It's used for the permanent storage of information. It also possesses random access property. Information can not be written into a ROM by the users/programmers. In other words the contents of ROMs are decided by the manufactures.

The following types of ROMs are listed below :

(i) **PROM** : It's programmable ROM. Its contents are decided by the user. The user can store permanent programs, data etc in a PROM. The data is fed into it using a PROM programmer.

(ii) **EPROM** : An EPROM is an erasable PROM. The stored data in EPROM's can be erased by exposing it to UV light for about 20 min. It's not easy to erase it because the EPROM IC has to be removed from the computer and exposed to UV light. The entire data is erased and not selected portions by the user. EPROM's are cheap and reliable.

(iii) **EEPROM (Electrically Erasable PROM)** : The chip can be erased & reprogrammed on the board easily byte by byte. It can be erased within a few milliseconds. There is a limit on the number of times the EEPROM's can be reprogrammed, i.e.; usually around 10,000 times.

Flash Memory : It's an electrically erasable & programmable permanent type memory. It uses one transistor memory cell resulting in high packing density, low power consumption, lower cost & higher reliability. It's used in all power, digital cameras, MP3 players etc.

Programmable logic array (PLA):-

A programmable logic array (PLA) is a kind of programmable logic device used to implement combinational logic circuits. The PLA has a set of programmable AND gate planes, which link to a set of programmable OR gate planes, which can then be conditionally complemented to produce an output.

Programmable Array Logic (PAL) is a family of programmable logic device semiconductors used to implement logic functions in digital circuits introduced by Monolithic Memories. PAL devices consisted of a small PROM (programmable read-only memory) core and additional output logic used to implement particular desired logic functions with few components

References:-

1. www.ece.gmu.edu
2. www.uotechnology.edu
3. www.verticalhorizons.in
4. Morris Mano “Digital electronics”
5. R.P Jain “Modern Digital electronics”